

Contents

PREFACE xv

LIST OF TABLES xvii

CHAPTER 1 Introduction 1

Sources 2

Lab Supplies 2

AC Mains 3

Batteries 4

Solar Cells 6

Loads 7

High Speed Requirements 7

Low Noise Requirements 8

Batteries, Again 10

Telephones 11

Fluorescent Tubes 12

Other Converters 13

Safety 13

CHAPTER 2 Practical Selection of Topology 17

Introduction: There Are Hundreds of Topologies! 17

General Considerations 18

Step-Up or Step-Down 18

Practical Limits on Duty Cycle 18

How Many Outputs? 19

Isolation 19

EMI	19
Bipolar versus MOSFET versus ?	20
Continuous and Discontinuous	20
Synchronous Rectification	21
Voltage Mode versus Current Mode	22
Conclusions	22
The Buck Topology	22
Limitations	23
Gate Drive Difficulties	23
The Flyback	25
Two Kinds	25
Name Confusion with Boost	26
Continuous versus Discontinuous	27
Capacitor Limitations	27
Power Limits	27
Practical Limits on Number of Outputs	28
The Buck–Boost	28
Limitations of the Buck-Boost	29
The Forward	29
Minimum Load	30
Leakage Inductance	30
Summary	31
The Push–Pull	31
Voltage-Fed	31
Current-Fed	32
Transformer Utilization	33
Resonant Converters and Soft-Switching Converters	33
The Difference between Resonant and Soft-Switching Converters	33
Why You Should <u>Not</u> Use Resonant Converters	34
Why You <u>Should</u> Use Soft-Switching Converters	34
Compound Converters	35
When to Use Them	36
References	36

CHAPTER 3 Practical Selection of Components 37

Introduction	37
Resistors	38
Values	38
Types of Resistor	38
Tolerance	39
Selecting Ratios	39
Maximum Voltage	39
Temperature Coefficient	39
Power Rating	39
Pulse Power	40
Rheostats: A What?	40

Noninductive Wirewound Resistors	42
Shunts	42
Using a Trace as a Resistor	43
Capacitors and their Usage	43
Types of Capacitors	43
Standard Values	44
Tolerance	44
ESR and Power Dissipation	44
Aging	45
dV/dt	45
Putting Caps in Series	46
Schottky Diodes	46
Rectifier Diodes	47
Reverse Recovery	47
Is Faster Better?	48
Transistors: BJTs	48
Pulse Current	48
How Much Beta Can I Get?	49
Don't Forget Collector Leakage Current	49
Emitter-Base Zenering—Is It Bad?	49
Fast Turnoff	49
Transistors: MOSFETs	50
Don't Confuse JFETs and MOSFETs	50
p-Channel and n-Channel	50
Bidirectional Conduction	50
Calculating Losses: Conduction Loss	51
Calculating Losses: Gate Charge Loss	51
Calculating Losses: Switching Loss	51
The Need for Gate Resistors	52
Maximum Gate Voltage	52
Op Amps	53
Offsets: Input Offset Voltage	53
Offsets: Input Offset Current	53
Offsets: Input Bias Current	54
What to Do About Offsets	54
Limits on Large Resistances	54
Gain Bandwidth	56
Phase Shift	56
Slew Rate	56
Comparators	57
Hysteresis	57
Output Saturation Voltage	58
References	58

CHAPTER 4 Practical Guide to Instrumentation 59

Introduction	59
Calculators and Calculations	59

How Many Digits? 59
Do I Care? 60
A Closely Related Problem 60
One More Problem to Avoid 61
DVMs and Other Meters 61
Accuracy versus Precision 61
Averaging 61
How to Filter a DVM 62
Measuring RMS and DVM Bandwidth 62
Measuring Efficiency: Cross-Calibration 63
Where to Put the Probes 63
Measuring Very Low Resistances 64
Using a Shunt for $I > 10A$ 64
How to Use a DVM to Measure a MOSFET 65
Electronic Loads 65
Why Is My Stable Converter Oscillating? 65
Minimum Input Voltage 66
Oscilloscopes 66
Aliasing 66
Network Analyzer 67
Step-by-Step Instructions 67
Nyquist Plots 69

CHAPTER 5 Practical Design of Magnetics 71

Fundamentals of Magnetics 71
Introductory Comments 71
Ampere's Law 72
Faraday's Law 72
About Inductance 73
Units Confusion 74
Weird Words: The Three R's 75
The Ideal Transformer 76
What About a Flyback "Transformer"? 77
Real Transformers 78
Core Materials 80
Saturation 80
Other Core Limitations 82
Optimum Design 83
Practical Design of a DC Inductor 83
Core Selection 84
First Try 84
Second Try 88
Selecting the Wire 89
Calculating the Resistance 90
Power Loss 92
Temperature Dependence 94
Conclusion 95

Practical Design of a Flyback Transformer	95
Equations Governing the Flyback	95
Selecting a Core Material Type	97
Core Selection	98
Selecting Core Material	98
Selecting the Gap	98
Core Loss	104
How Did He Read That Little Graph?	104
Can I Get Lower Core Losses by Lowering the Switching Frequency?	106
Winding Losses	107
Do I Need to Worry About Skin Effect?	108
Copper Loss and Total Transformer Loss	109
Flux Density: Two Formulas?	110
Practical Design of a Forward Transformer	110
Practical Design of a Current Transformer	113
Tips for Designing Manufacturable Magnetics	115
Wire Gauge	115
Wire Gauge Ratio	116
Toroid Winding Limits	116
Tape versus Wire Insulation	116
Layering	117
Number of Windings	117
Potting	117
Specs	118
Concluding Comments	118
References	119

CHAPTER 6 Practical Feedback Design 121

Introduction	121
Refresher	121
Logarithms and dB	121
Complex Numbers	122
Complex Functions	123
What Is a Transform?	124
Two Transforms	124
What's the Difference?	125
Transform of C and L	125
Transfer Functions	126
What Is a Transfer Function and Who Cares?	126
Composition Law for Transfer Functions	126
There's No Such Thing as a (Useful) Transform of a Nonlinear System!	128
Basic Control Theory	128
Bode Plots	129
Requirement for Stability	130
How Much Phase Margin Is Enough?	132
Gain Margin?	133

About Conditional Stability	134
Small- versus Large-Signal Stability	134
How to Stabilize a Voltage Mode Buck Converter	135
How to Measure Open Loop Response	136
Venable's <i>K</i> -Factor Paper	138
Practical Considerations	142
Other Comments	142
How to Measure Closed Loop Response	143
How to Measure It: Transformer Method	144
How to Measure It: The Mixer Method	144
Converter Closed Loop	145
How NOT to Measure a Loop	146
A Better Method of Measuring the Open Loop	147
What If the Noninverting Pin of the Error Amp Isn't Available?	149
Current Mode Control	149
Theory	149
A Limitation of Current Mode Control	150
Slope Compensation	150
How to Compensate a Current Mode Controller	152
Can I Measure the Current Loop?	152
Average Current Mode Control	152
Non-Minimum-Phase Systems	153
Nyquist Plots	154
Some Concepts of System Stability	155
Input and Output Impedance	155
Converter Output Impedance	158
Two Stable Converters Can Make an Unstable System!	159
Example of an Unstable System	161
Some Thoughts on the Role of Simulations	161
References	163

CHAPTER 7 Practical Design of Control and Monitoring Circuitry 165

Control Circuitry	165
Start-Up	165
Soft Start	167
Sequencing	168
Feedback	168
Current Limiting	170
Switching Frequency	171
Synchronization	171
Monitoring Circuitry	172
How to Monitor Voltage	172
Voltage References	173
How to Monitor a Negative Supply Without a Negative Rail	173
Why You Should Always Use Hysteresis on Comparators	174
Resistors and Shunts	175
Differential Amplifiers	175

Compensating Shunt Inductance 177
Fail Should Be Low 178
Driving That Red LED 178

CHAPTER 8 Practical Efficiency and Thermal Management 179

Efficiency 179
 Definition 179
 Why Is Efficiency Important? 179
 Modules 180
 90% Is Doing Great! 180
 Example Calculation 1 181
 Example Calculation 2 188
 Improving Efficiency 189
Thermal Management 190
 Component Life versus Temperature 190
 Modules 191
 MIL-HDBK-217 192
 MIL-HDBK-217: Example 192
 MIL-HDBK-217: Discussion 194
 Temperature Calculation 195
 Heat Sinks, etc. 196
 FEA 197
References 197

CHAPTER 9 Practical EMI Control 199

An Overview 199
 Radiated and Conducted 200
 What to Do About Radiated Noise 200
 What Kind of Box Material? 201
 Common Mode versus Normal Mode 201
 Return versus Ground 202
 Military versus Commercial Measurements 203
How Can I Separate CM from NM? 203
Where Does the Noise Come From? 204
 Switching Waveforms 205
 Capacitive Coupling 205
Concepts of Layout 207
 Signal Ground versus Power Ground 207
 Grounding a High Current Driver; Ground Islands 209
 What If the Device Has a Signal Input But No Signal Ground? 210
 Where to Put the Current Transformer 210
 Feedback Lines 211
 Further Layout Tips 212
Low Frequency Filtering 212
 The Basics 212
 Normal Mode Filters 213

Commercial versus Military	213
Selecting the Values	214
Common Mode Filters	214
Selecting the Values	215
Caps and Inductors and Their Limits	216
MOVs Have Capacitance	216
Two for the Price of One	216
You Can't Get 100dB Attenuation!	217
High Frequency Filtering	217
Where Should I Use Beads?	217
Feedthroughs	218
Some Other Topics	218
Noise Estimation	218
Optimal Filtering	219
Optimal Military EMI-Filter Design	219
Converter Stability versus EMI Filtering	222
References	223

CHAPTER 10 Practical Worst-Case Analysis 225

Introduction	225
The Purpose of Worst-Case Analysis	225
How Do You Do WCA?	225
The Purpose of Stress Analysis	226
RMS versus Worst Case	227
Mathematics versus Simulation	227
Monte Carlo? Sensitivity Analysis?	228
An Exhausting Example	228
The Circuit	229
Properties to be Analyzed	229
Table Evaluation Techniques	230
Worst-Case Analysis: Comparator Trip Levels	233
Worst-Case Analysis: The BJT Is Normally Off	234
Worst-Case Analysis: How Long Until the PWM Is Turned Off?	235
Stress Analysis	236
Conclusions	238
Some Concluding Thoughts	238

APPENDIX 1 List of Acronyms Used in the Book and Some Symbols 239

APPENDIX 2 Data Sheets for Worst-Case Analysis 241

INDEX 259

ABOUT THE AUTHOR 267